



KD Campus Pvt. Ltd

2007, OUTRAM LINES, 1ST FLOOR, OPPOSITE MUKHERJEE NAGAR POLICE STATION, DELHI-110009

Answer-key & Solution

SSC JE (Circuit Theory)
Date 15.07.2017

1. C	13. B	25. C	37. D	49. A	61. B	73. B	85. C
2. B	14. D	26. D	38. C	50. D	62. B	74. B	86. B
3. D	15. A	27. B	39. B	51. B	63. D	75. A	87. C
4. A	16. D	28. A	40. C	52. A	64. C	76. D	88. B
5. D	17. A	29. B	41. C	53. C	65. D	77. D	89. C
6. B	18. A	30. C	42. A	54. A	66. B	78. C	90. A
7. A	19. D	31. A	43. A	55. C	67. A	79. D	
8. D	20. B	32. A	44. B	56. B	68. C	80. A	
9. D	21. C	33. B	45. C	57. A	69. A	81. A	
10. D	22. B	34. A	46. A	58. A	70. A	82. D	
11. D	23. A	35. C	47. B	59. A	71. A	83. C	
12. B	24. A	36. C	48. A	60. B	72. B	84. A	

Note : *If your opinion differ regarding any answer, please message the mock test and Question number to 9560620353*

Note : *If you face any problem regarding result or marks scored, please contact : 9313111777*

SOLUTION


51.(B) At resonance

$$I = I_R = 1 \text{ mA}$$


$$|I_R + I_L| = \sqrt{I_R^2 + I_L^2} = \sqrt{1^2 + I_L^2} > 1 \text{ mA}$$

$$|I_R + I_L| > 1 \text{ mA}$$

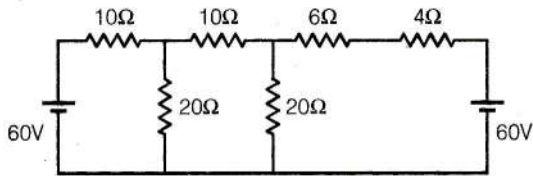52.(A) Using source transformation, the circuit is redrawn.




Further,

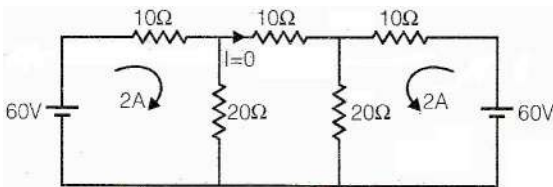

It is a symmetrical network.
So, $I = 0$.

53.(C)

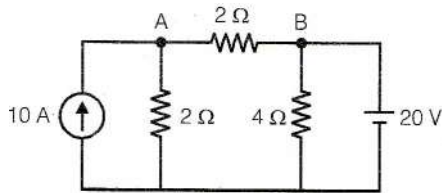

Applying KCL at node A

$$\frac{V_A}{2} + \frac{V_A - V_B}{2} = 10$$


$$\Rightarrow 2V_A - V_B = 20 \quad \dots(i)$$

But, $V_B = 20 \text{ V}$

Hence current through branch AB

$$= \frac{V_A - V_B}{2} = \frac{20 - 20}{2} = 0$$

56.(B)

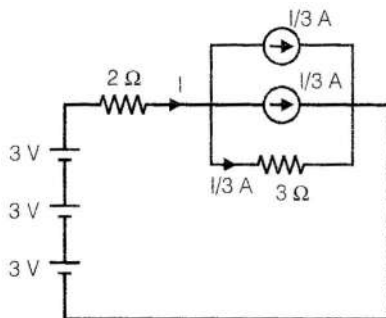

Applying KVL to mesh


$$-3 - 3 - 3 + 2I + 3\frac{I}{3} = 0$$

$$3I = 9 \Rightarrow I = 3 \text{ Amp.}$$

So voltage developed across 3Ω


$$= 3\frac{I}{3} = 3\text{V}$$

57.(A)

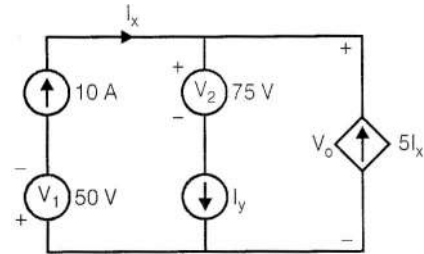

According to Tellegen's theorem, net power developed in any circuit is always zero.

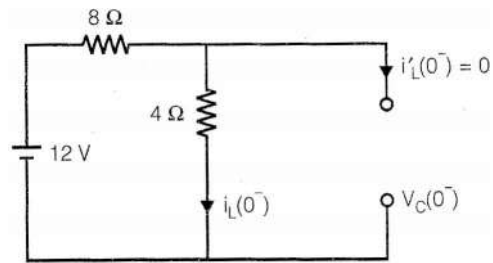
58.(A) At $t = 0^-$ circuit is in steady state; so it can be redrawn as



$$i_L(0^-) = \frac{12}{12} = 1\text{A}$$

$$V_C(0^-) = 4 \times 1 = 4\text{V}$$

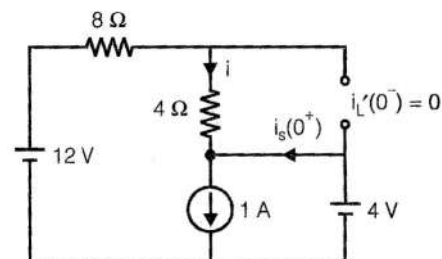Now at $t = 0^+$ circuit can be redrawn as



$$\text{Now } i = \frac{12 - 4}{8 + 4} = \frac{3}{2} \text{ A}$$

$$\text{But, } i + i_s(0^+) = 1$$

$$\therefore i_s(0^+) = 1 - i = 1 - \frac{3}{2}$$

$$\Rightarrow i_s(0^+) = \frac{1}{3} \text{ A}$$

59.(A) Applying KVL, $20 - 5I - 5 \left(1 + \frac{V_1}{5}\right) = 0$

$$20 - 10I - 20 = 0$$

$$\Rightarrow I = 0$$

\therefore Only dependent source acts.

$$\frac{V_1}{5} = 4 \text{ A}$$

Power delivered

$$= I^2 R = 16 \times 5 = 80 \text{ W}$$

60.(B) Average power is same as RMS power.

$$P = I_{rms}^2 R = \left(\frac{5}{\sqrt{2}}\right)^2 \times 4 = \frac{25}{2} \times 4 = 50 \text{ W}$$

$\frac{25}{2} \times 4 = 50 \text{ W}$ (Power is consumed only by resistance) i.e by real part of impedance.

64.(C) Code

Red - 2

Orange - 3

Orange - 3

equivalent resistance (R_{eq}) = 23×10^3

Source voltage = 50V

$$= \frac{50}{23 \times 10^3} = \frac{50}{23} \text{ mA}$$

$$\Rightarrow 2.17$$

$$\Rightarrow 2.2 \text{ A Approximate}$$

65.(D) $I_{av} = ?$

for metallic wire,

electron per second = 10^{20} e/s

$q = it$.

For $t = 1 \text{ sec}$

$q = i$


$$q = ne = 10^{20} \times 1.6 \times 10^{-19}$$

$$\Rightarrow q = 10 \times 1.6$$

$$\Rightarrow q = 16 \text{ coulomb}$$

$$i = q = 16 \text{ amp} \quad (t = 1)$$

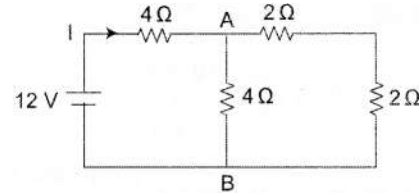87.(C) In order to calculate the voltage across 4Ω resistor, first we will calculate the current in 4Ω resistor due to voltage source, due to finding this calculate I as shown in the figure.



$$I = \frac{V}{R_{eq}}$$

$$R_{eq} = 4 + 4 \parallel (2 + 2) = 4 + 2 = 6\Omega$$

$$\text{so, } I = \frac{12}{6} = 2 \text{ amp.}$$

Now, the current in branch AB

$$= I \times \frac{4}{4 + 4} = \frac{2 \times 4}{8} = 1 \text{ amp.}$$

so, voltage drop across $4\Omega = 1 \times 4 = 4 \text{ V}$

88.(B) In a series R-C circuit

$$V_C = 60 \text{ V}$$

$$V_R = 80 \text{ V}$$

Input voltage $V_{in} = ?$

from the circuit

$$|V_{in}| = \sqrt{V_C^2 + V_R^2}$$

$$\Rightarrow |V_{in}| = \sqrt{(60)^2 + (80)^2} \Rightarrow |V_{in}| = \sqrt{3600 + 6400}$$

$$\tan \theta = \frac{V_C}{V_R} = \frac{60}{80} = \frac{3}{4}$$

$$\theta = \tan^{-1}\left(\frac{3}{4}\right) = +36.86 = 37^\circ \text{ C}$$

$$V_{in} = |V_{in}| \angle -\theta$$

$$V_{in} = 100 \angle -37^\circ \text{ C}$$

90.(A) $V = 10 \angle 15^\circ$; $I = 2 \angle -45^\circ$

Active power

$$= V_{rms} \cdot I_{rms} \cos \theta = \frac{10 \times 2}{2} = 10 \text{ Watt}$$

Reactive power = $V_{rms} I_{rms} \sin \theta$

$$= \frac{10 \times \sqrt{3} \times 2}{2} = 17.3 \text{ VAR}$$